

DELHI TECHNOLOGICAL UNIVERSITY



EE 313

LIC LAB REPORT

Submitted to:

Prof. Pragati Kumar

Submitted by:

Abhigyan Adarsh

2K19/EE/005

CONTENTS

S.No.	Experiment	Pg.No.
1.	To design and implement the different types of amplifiers using IC 741: Inverting, Non-Inverting & Voltage Follower	3
2.	To design and implement using IC 741: Integrator & Differentiator	8
3.	To design and implement a square wave generator using IC-741 (astable multivibrator)	13
4.	To design and implement a Schmitt trigger with inverting and non-inverting transfer characteristics using IC-741	15
5.	To design and implement the following types of relaxation oscillator: Triangular & Saw Tooth	18
6.	To design and implement a Wein Bridge Oscillator (WBO).	21
7.	Implementation of a 2nd order low pass filter.	23
8.	Implementation of a 2nd order high pass filter.	25
9.	To design and implement a GIC (Generalized impedance converter) based 2nd order band pass filter using μA 741.	28


EXPERIMENT 1

Aim : To design and implement the following types of amplifiers using IC 741

- a. Inverting
- b. Non-inverting
- c. Voltage follower

1. Inverting Amplifier

a. Circuit Diagram:

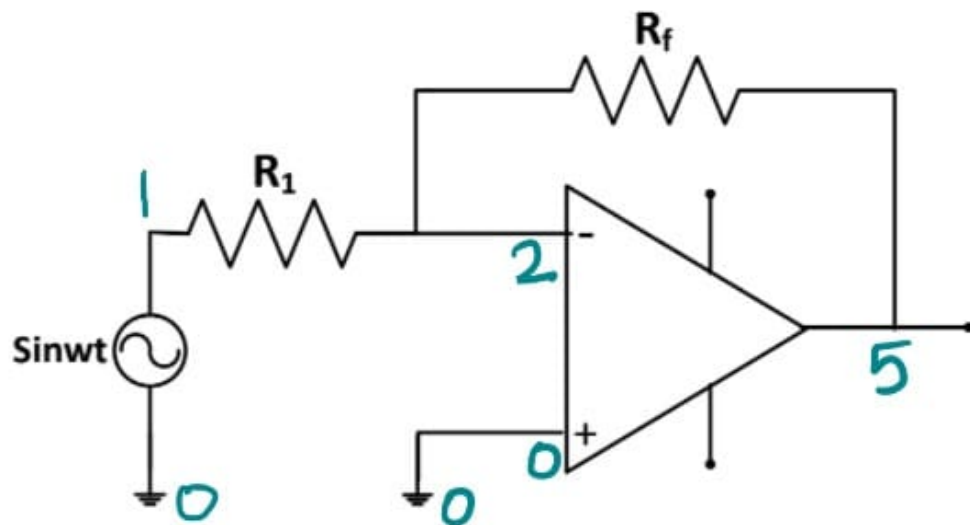

b. Netlist code


```
*Exp-1.1 a Inverting Amplifier
X1 0 2 3 4 5 ua741
V1 0 1 AC 10m sin(0 8m 1k)
R2 5 2 10K
R1 2 1 1K
Vp 3 0 DC 12
Vn 0 4 DC 12

* Analysis setup *
.tran 0 5m
.probe


.ac dec 100 1 100Mega
.probe
```

c. Simulation

Transient Analysis

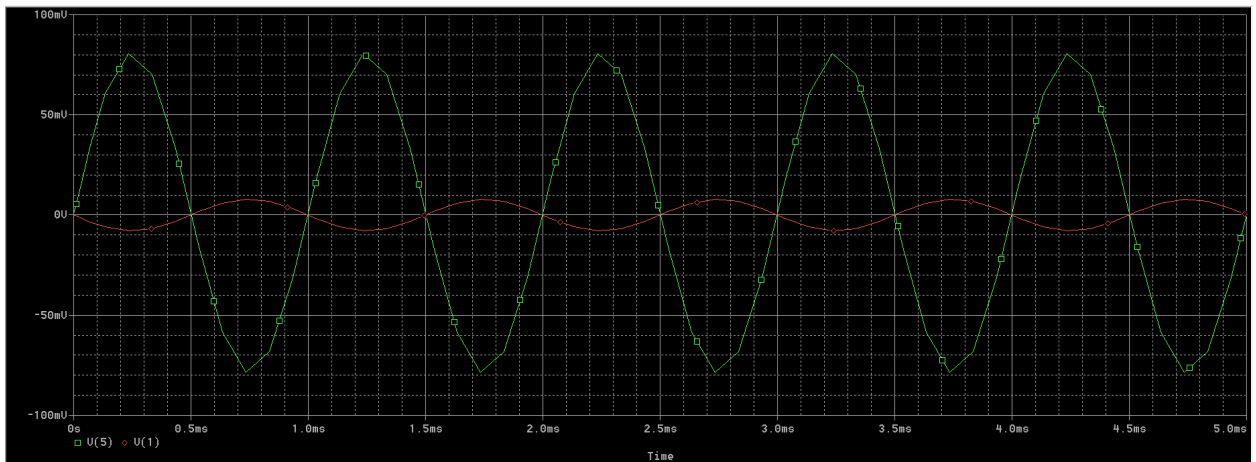


AC Analysis

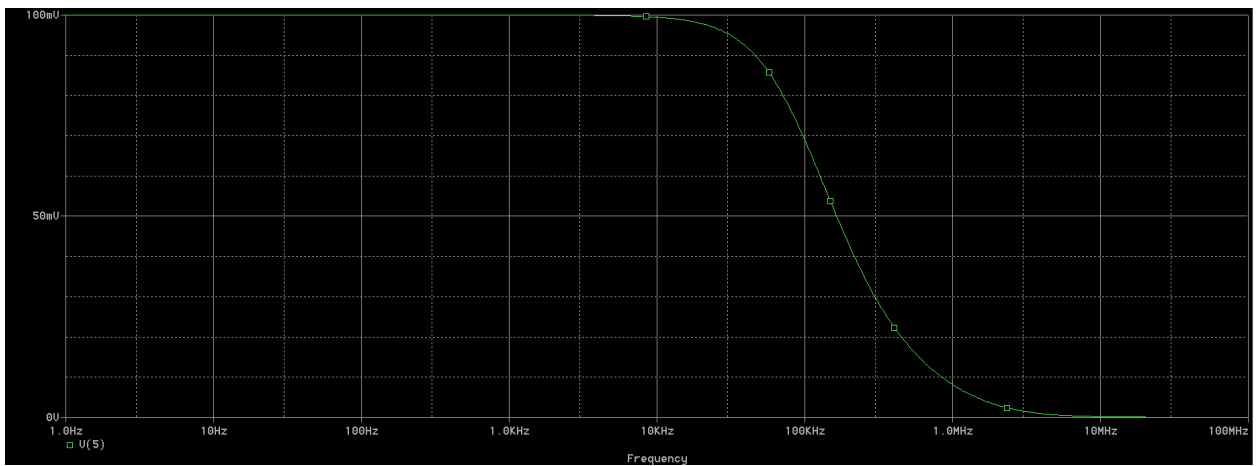

2. Non-Inverting Amplifier


a. Circuit diagram

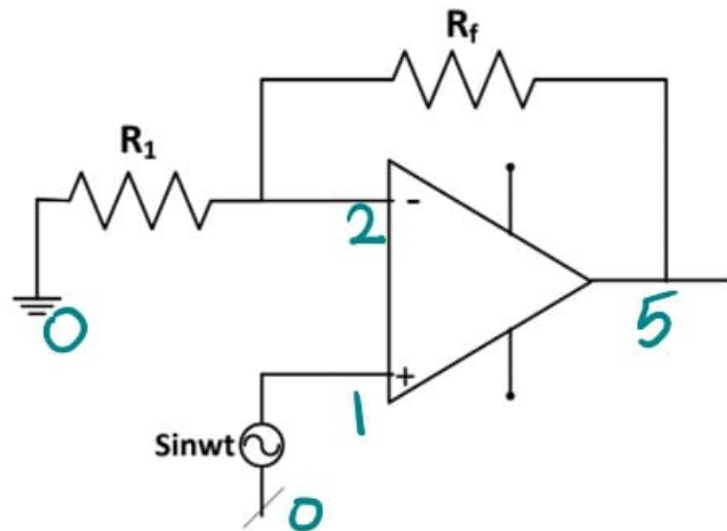


b. Netlist Code

```
*Exp-1.1 b Non-Inverting Amplifier
X1 1 2 3 4 5 ua741
V1 0 1 AC 10m sin(0 8m 1k)
R2 5 2 10K
R1 2 0 1K
Vp 3 0 DC 12
Vn 0 4 DC 12
* Analysis setup *
.tran 0 5m
.probe
.ac dec 100 1 100Mega
.probe
```

c. Simulation Transient Analysis

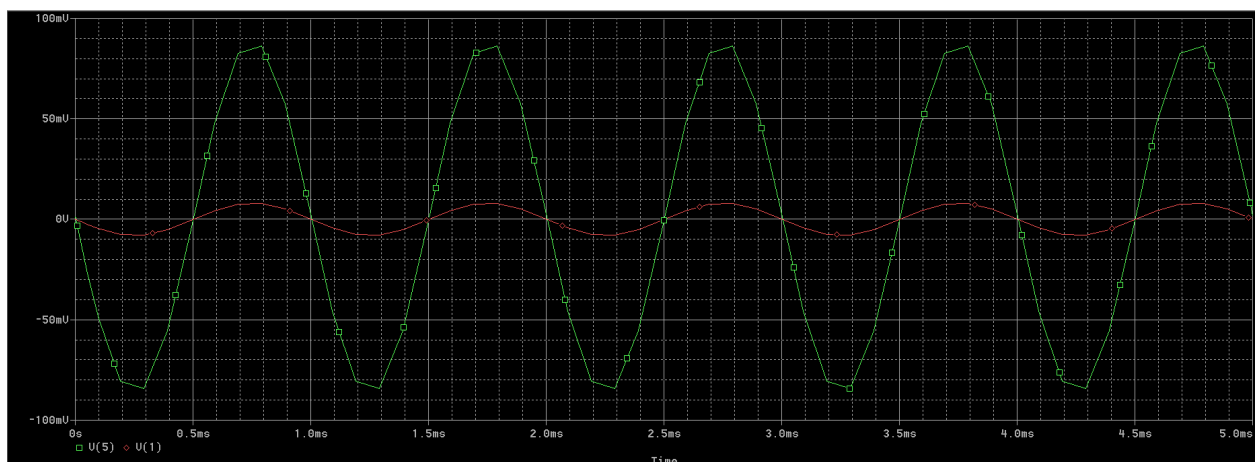


AC Analysis

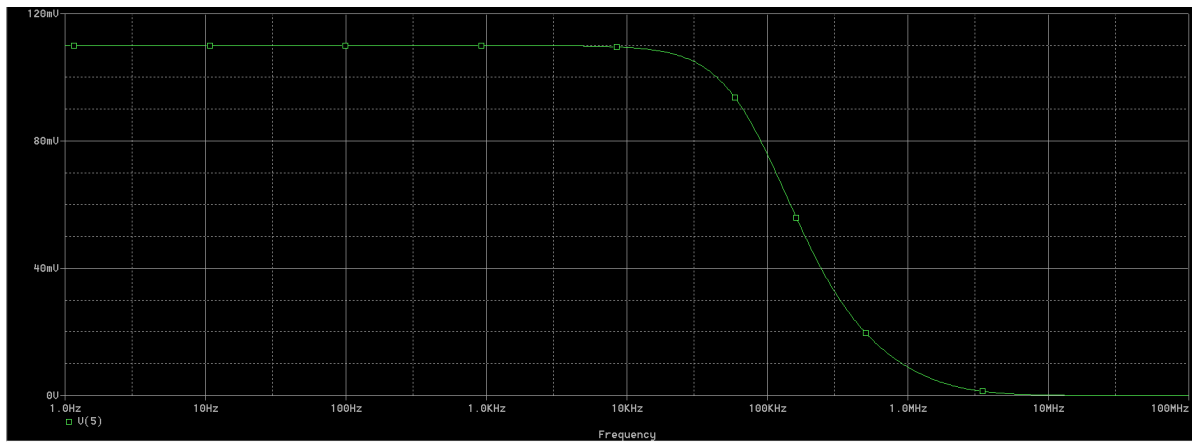

3. Voltage follower

a. Circuit diagram

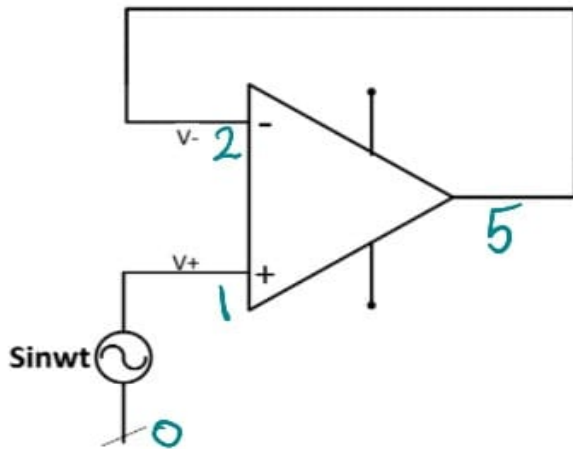


b. Netlist Code


```
*Exp-1.1 c Voltage Follower
X1 1 2 3 4 5 ua741
V1 0 1 AC 10m sin(0 8m 1k)
Vo 2 5 DC 0
Vp 3 0 DC 12
Vn 0 4 DC 12
* Analysis setup *
.tran 0 5m
.probe
.ac dec 100 1 100Mega
.probe
```

c. Simulation

Transient Analysis

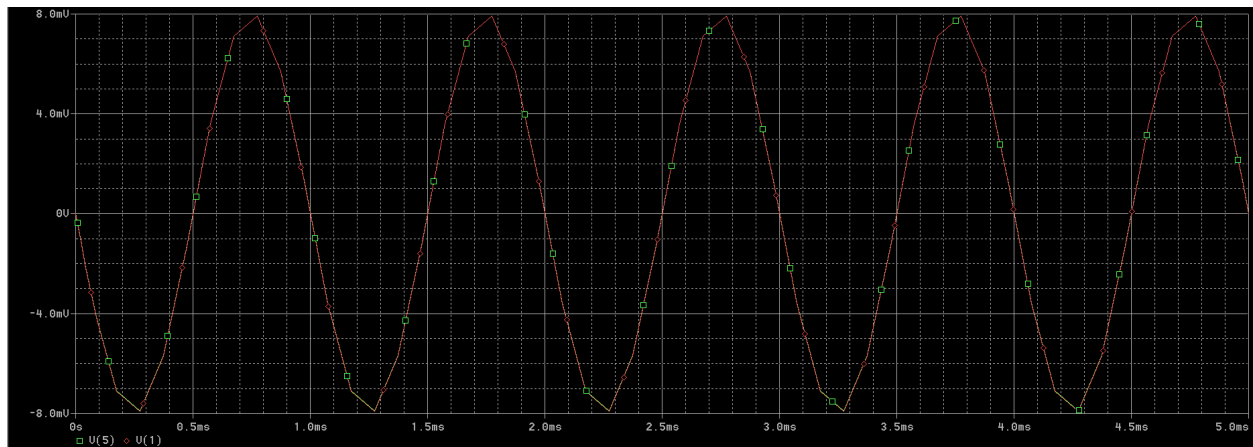

AC Analysis

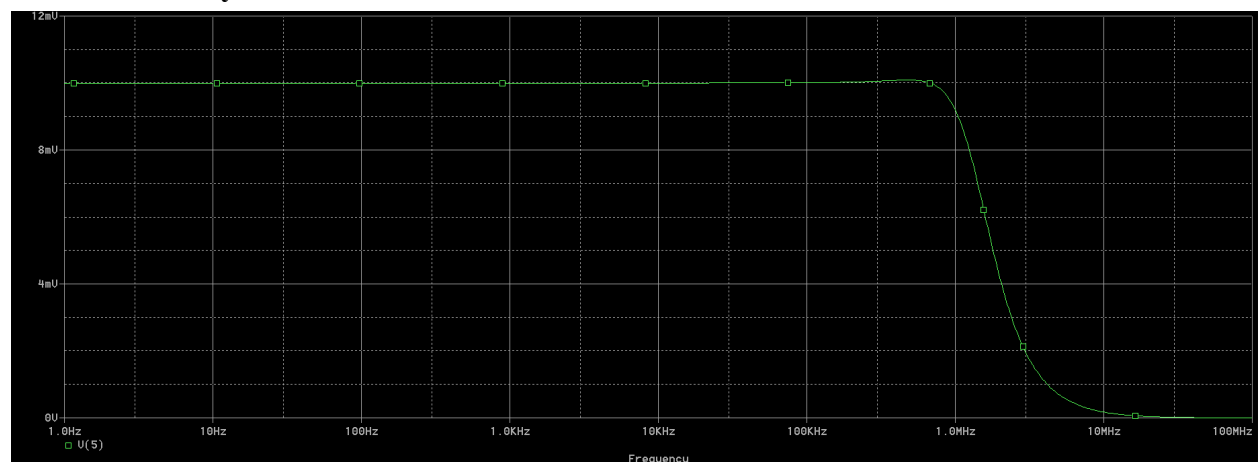

EXPERIMENT 2


Aim : To design and implement using IC 741

- 1) Integrator
- 2) Differentiator

1. Integrator

A. Ideal Integrator



a. Circuit Diagram

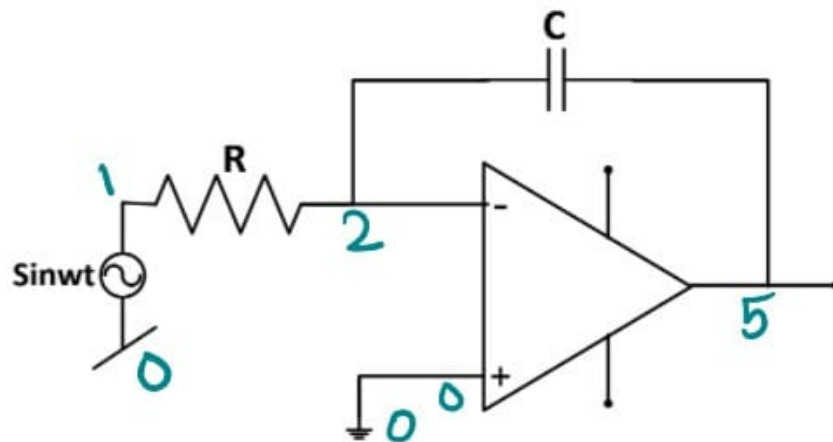

b. Netlist Code


```
*Exp-2 a Ideal Integrator
X1 0 2 3 4 5 ua741
*graph 1
V1 0 1 AC 10m sin(0 500m 1k)
*graph 2
V1 0 1 pulse(-500mv 500mv 0 0 0 1ms 4ms)
C 5 2 10n
R1 2 1 4k
Vp 3 0 DC 8
Vn 0 4 DC 8
* Analysis setup *
.tran 0 60m
.probe
.ac dec 100 1 100Mega
.probe
```


c. Simulation

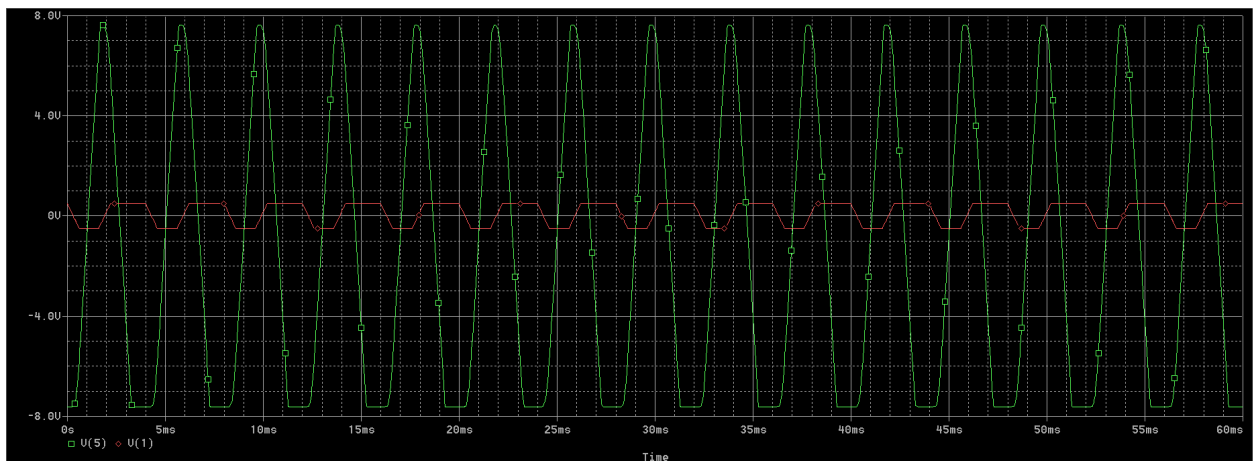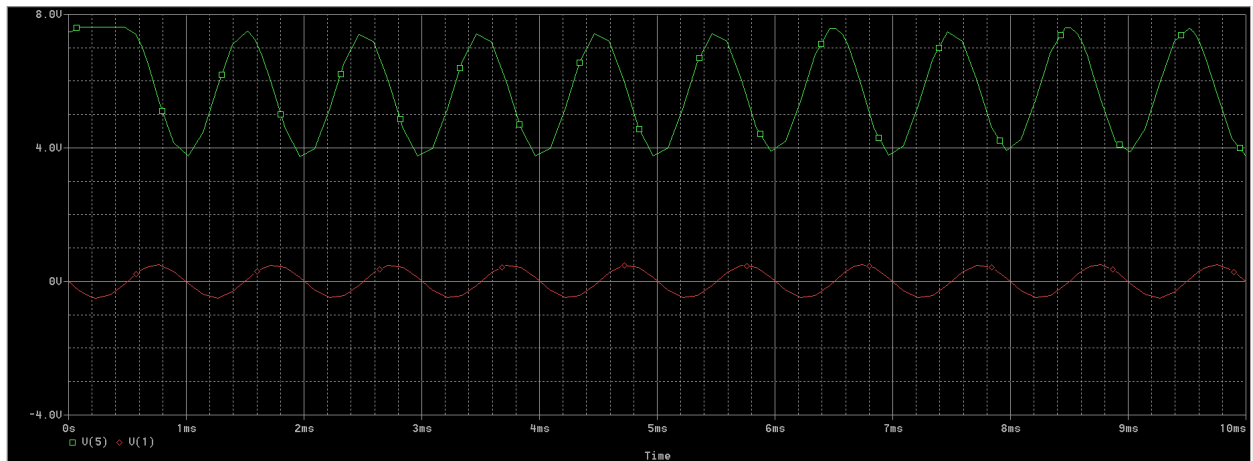

B. Lossy Integrator



a. Circuit Diagram

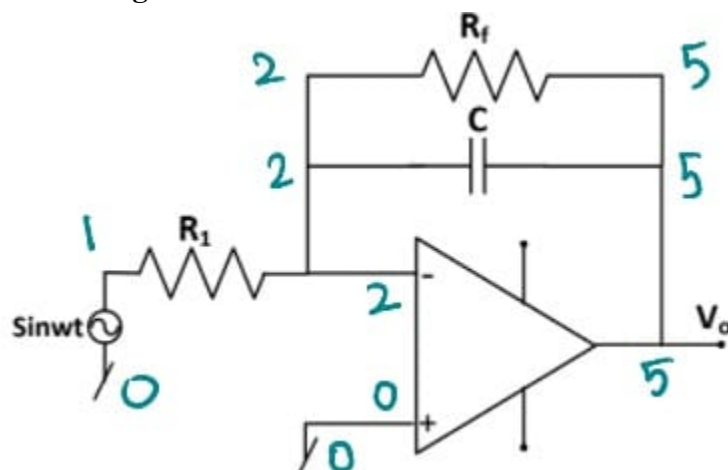

b. Netlist Code


```
*Exp-2 aii Lossy Integrator
X1 0 2 3 4 5 ua741
*graph 1
V1 0 1 AC 100m sin(0 10m 1k)
*graph 2
V1 0 1 pulse(-500mv 500mv 0 0 0 0.2ms 2ms)
C 5 2 10n
R1 2 1 2k
R2 2 5 10k
Vp 3 0 DC 8
Vn 0 4 DC 8
* Analysis setup *
.tran 0 30m
.probe
.ac dec 100 1 100Mega
.probe
```

c. Simulation

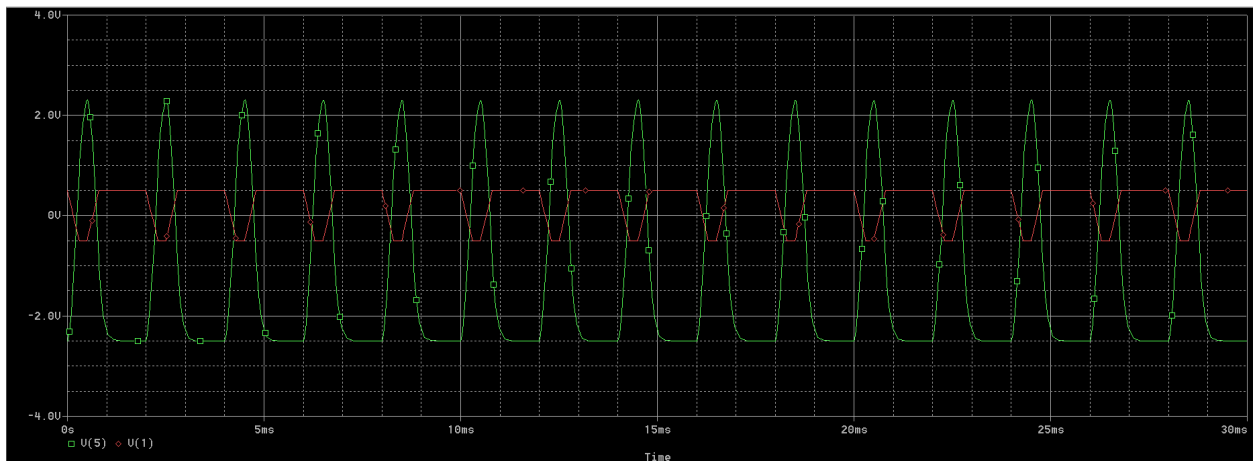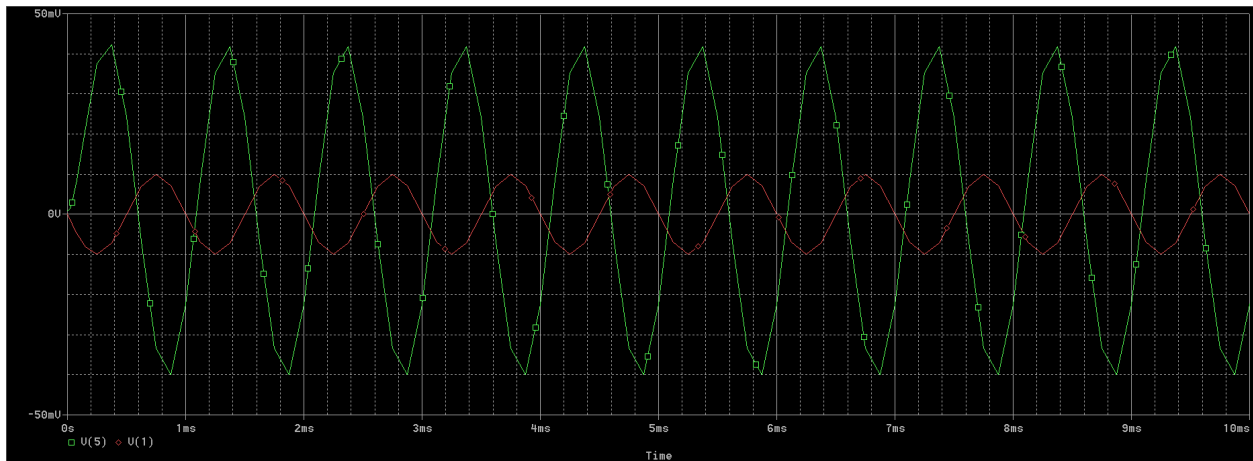

2. Differentiator

a. Circuit Diagram

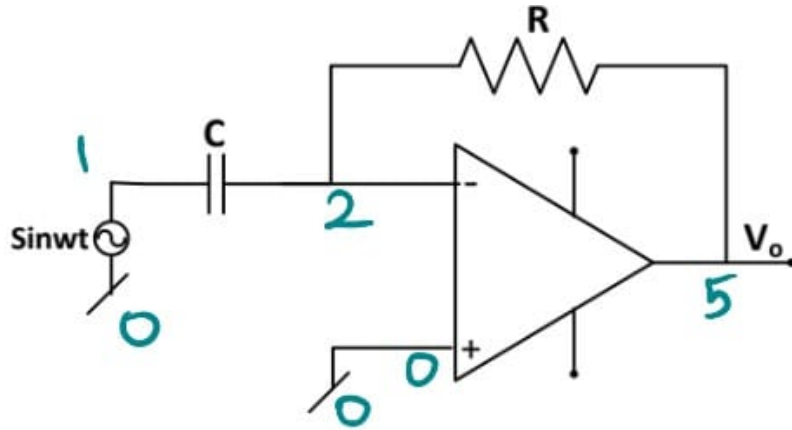



b. Netlist Code

```
*Exp-2 b Differentiator
X1 0 2 3 4 5 ua741
*graph 1
V1 0 1 AC 500m sin(0 8m 500k)
*graph 2
V1 0 1 pulse(-500mv 500mv 0 0 0 1ms 5ms)
C 1 2 100u
R 2 5 100k
Vp 3 0 DC 15
Vn 0 4 DC 15

* Analysis setup *
*graph 1
.tran 0 50u
*graph 2
.tran 0 50m
.probe

.ac dec 100 1 100Mega
.probe
```

c. Simulation

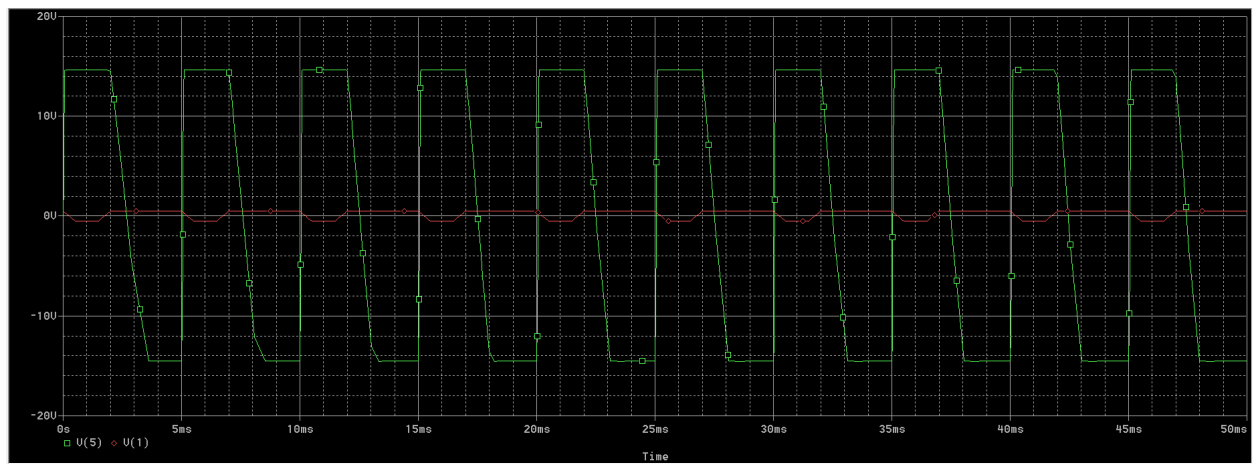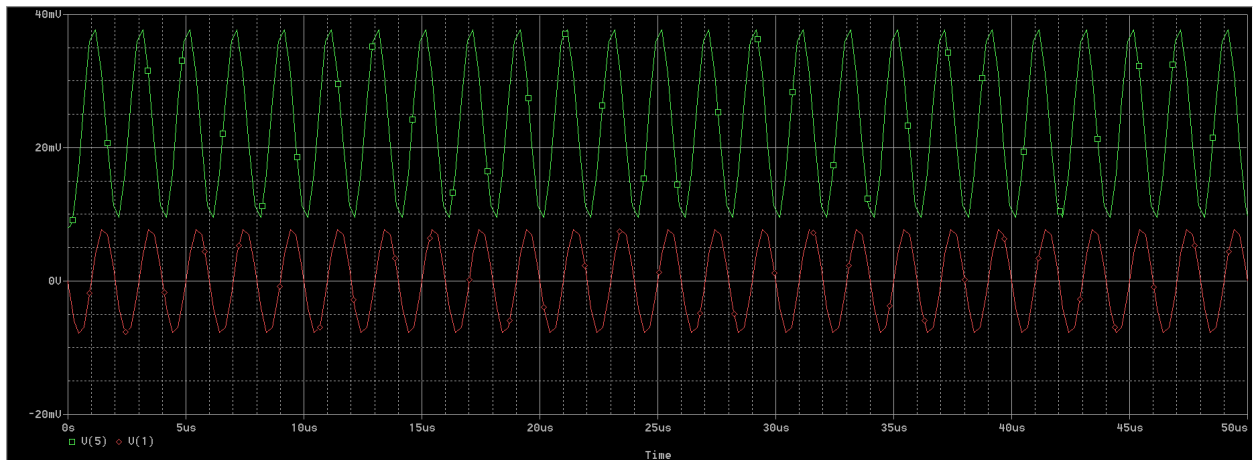

EXPERIMENT 3

Aim : To design and implement a square wave generator using IC-741 (astable multivibrator).

Design Procedure :

Given frequency = 100Hz

Therefore to design the square wave generator:

$$T = 2RC \ln(1+2R_1/R_2)$$

Where $T = 1/f = 1/100 = 10\text{ms}$

Let $R = 5\text{k}\Omega$

$$C = 1\mu\text{F}$$


hence, $2RC = 2 \times 5000 \times 0.000001 = .01$

now, $\ln(1+2R_1/R_2) = 1$ // to make $T = .01\text{s}$

On solving the above eqn : $R_2 = 1.164R_1$

Take $R_1 = 10\text{k}\Omega$ therefore, $R_2 = 11.64\text{k}\Omega$

Therefore, the value of components are :

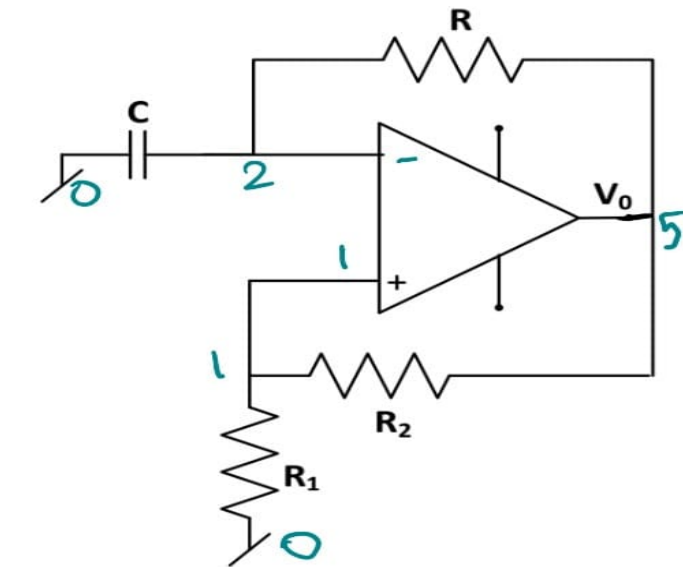

$R = 5\text{k}\Omega$

$C = 1\mu\text{F}$

$R_1 = 10\text{k}\Omega$

$R_2 = 11.64\text{k}\Omega$

($T = 10\text{ms}$ and frequency = 100Hz)

Netlist Code

```
*Exp-3 Square Wave Generator Astable Multivibrator  
X1 1 2 3 4 5 ua741
```

```
C 0 2 10n
```


```
R 2 5 10k  
R1 1 0 10k  
R2 1 5 10k
```

```
Vp 3 0 DC 10  
Vn 0 4 DC 10
```

```
* Analysis setup *  
.tran 0 5m  
.probe
```

```
.ac dec 100 1 100Mega  
.probe
```

Simulation

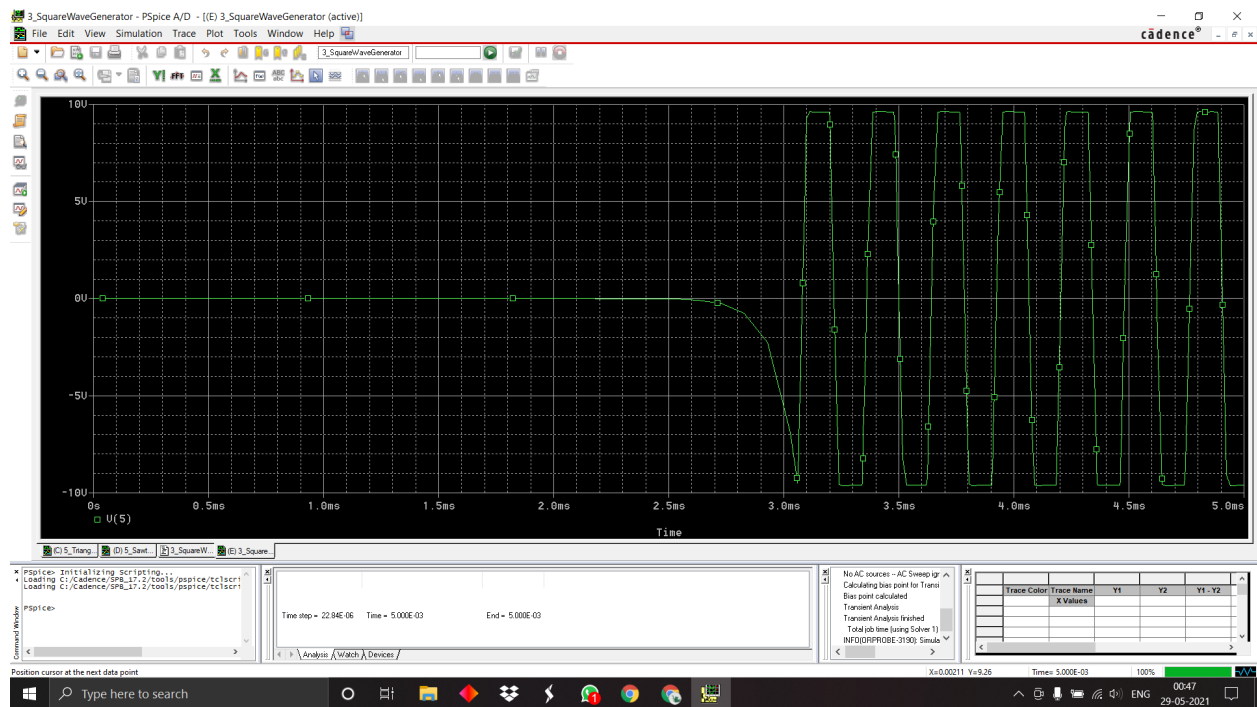


EXPERIMENT 4

Aim : To design and implement a Schmitt trigger with inverting and non-inverting transfer characteristics using IC-741.

1. Inverting Mode

a. Circuit Diagram

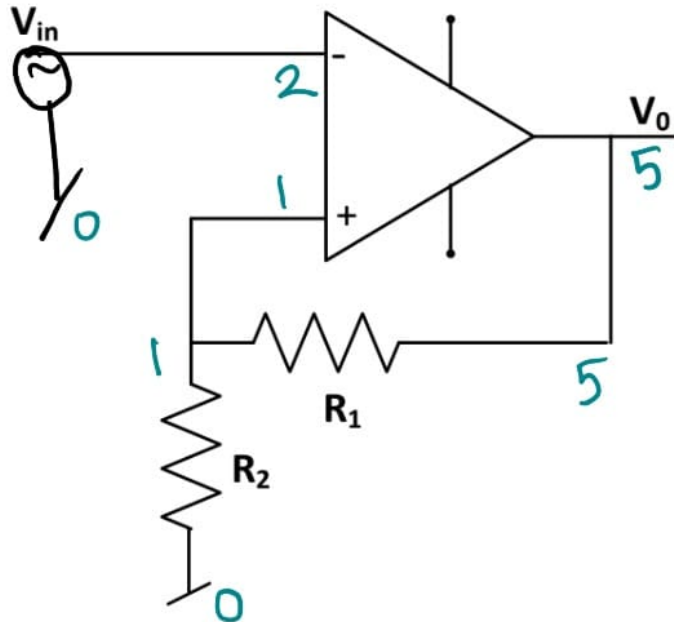

b. Netlist Code

```
*Exp-7 Schmitt Trigger IA Mode
X1 1 2 3 4 5 ua741


V1 0 2 AC 500m sin(0 10 159)

R1 1 5 10k
R2 1 0 10k

Vp 3 0 DC 10
Vn 0 4 DC 10


* Analysis setup *
.tran 0 100ms
.probe
```

c. Simulation

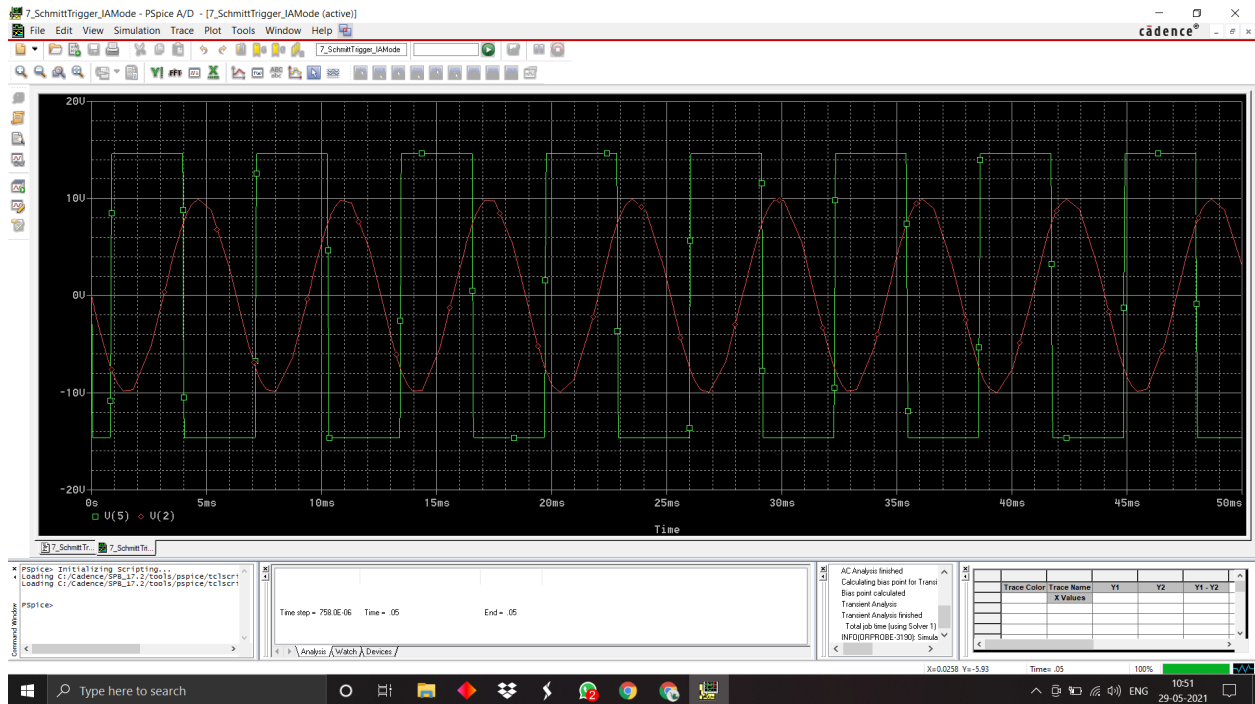

2. Non-Inverting Mode

a. Circuit Diagram

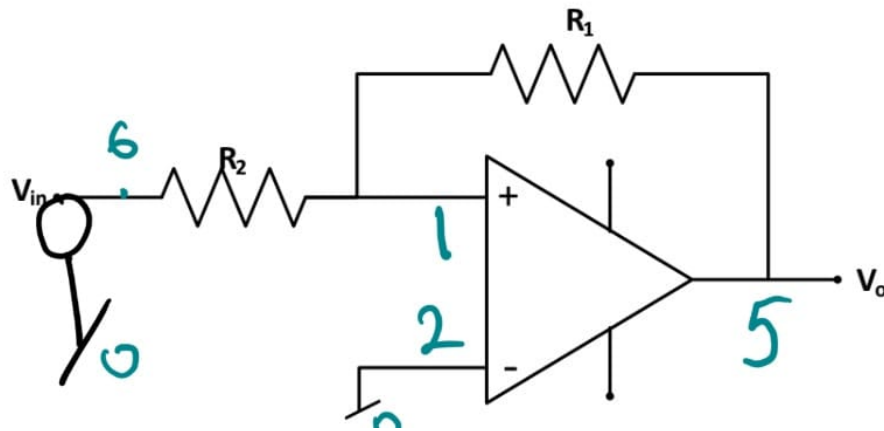

b. Netlist Code

*Exp-7 Schmitt Trigger NIA Mode

X1 1 0 3 4 5 ua741

V1 0 6 AC 500m sin(0 10 159)

R1 1 5 10k


R2 1 6 5.8k

Vp 3 0 DC 15

Vn 0 4 DC 15

```
* Analysis setup *  
.tran 0 50ms  
.probe
```

c. Simulation

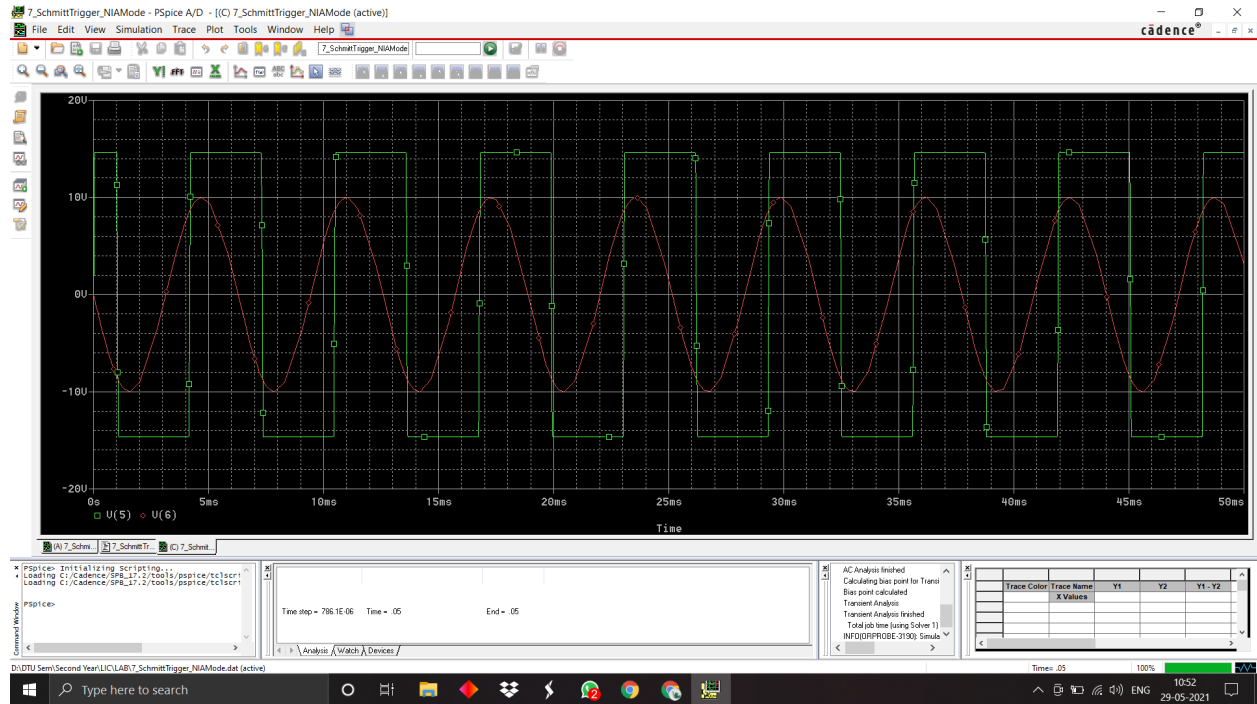


EXPERIMENT 5

Aim : To design and implement the following types of relaxation oscillators

- 1) Triangular
- 2) Rectangular

Triangular-wave and square-wave

a. Circuit Diagram

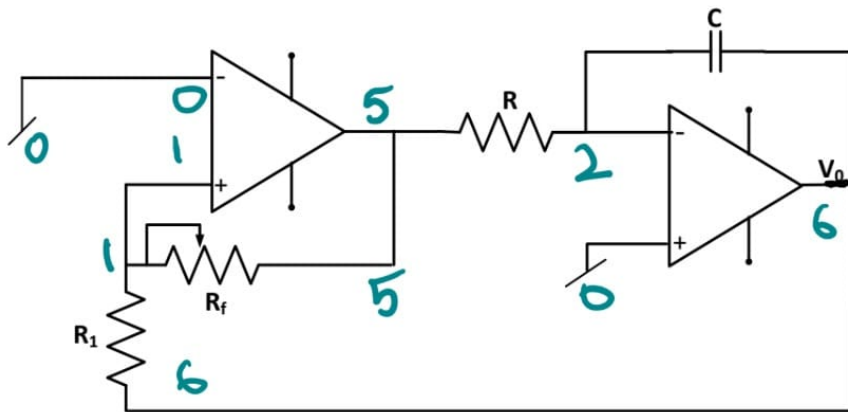

b. Netlist Code

```
*Exp-5 Triangular Wave Generator
```

```
X1 1 0 3 4 5 ua741
```

```
X2 0 2 3 4 6 ua741
```

```
C 6 2 0.05u
```

```
R2 2 5 10k
```

```
R1 1 6 10k
```

```
R3 1 5 40k
```

```
Vp 3 0 DC 15
```

```
Vn 0 4 DC 15
```

```
* Analysis setup *
```

```
.tran 0 10m
```

```
.probe
```

```
.ac dec 100 1 100Mega
```


```
.probe
```

c. Simulation



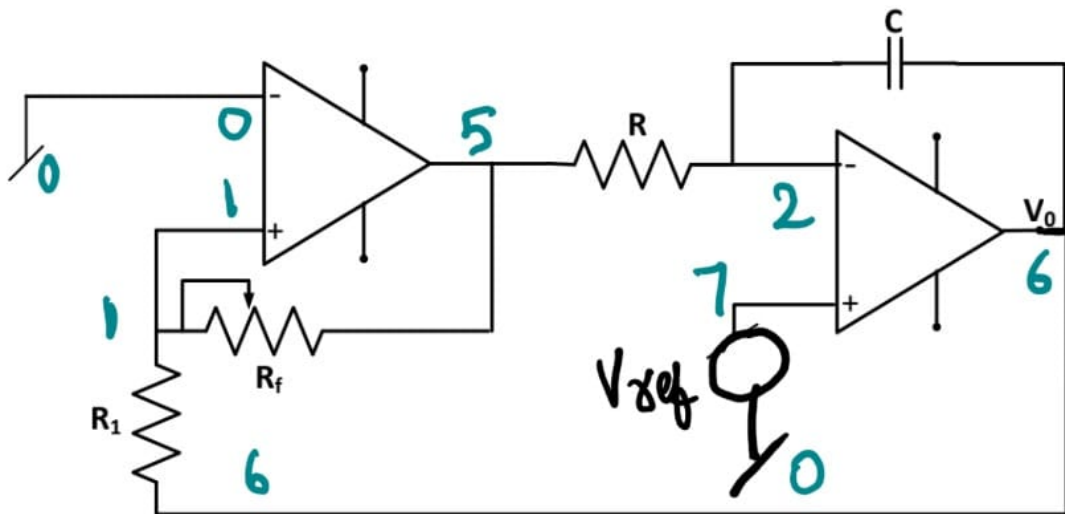2. Sawtooth wave and Square wave

Only add a 7V DC source at the non-inverting terminal of the second opamp.



a. Netlist Code

*Exp-5 Sawtooth Generator

X1 1 0 3 4 5 ua741

X2 0 2 3 4 6 ua741

C 6 7 0.05u

R3 1 5 40k

```
Vref 7 2 DC 7
```

Vp 3 0 DC 15

Vn 0 4 DC 15

* Analysis setup *


```
.tran 0 10m
```

```
.probe
```

```
.ac dec 100 1 100Mega
```

```
.probe
```


b. Simulation

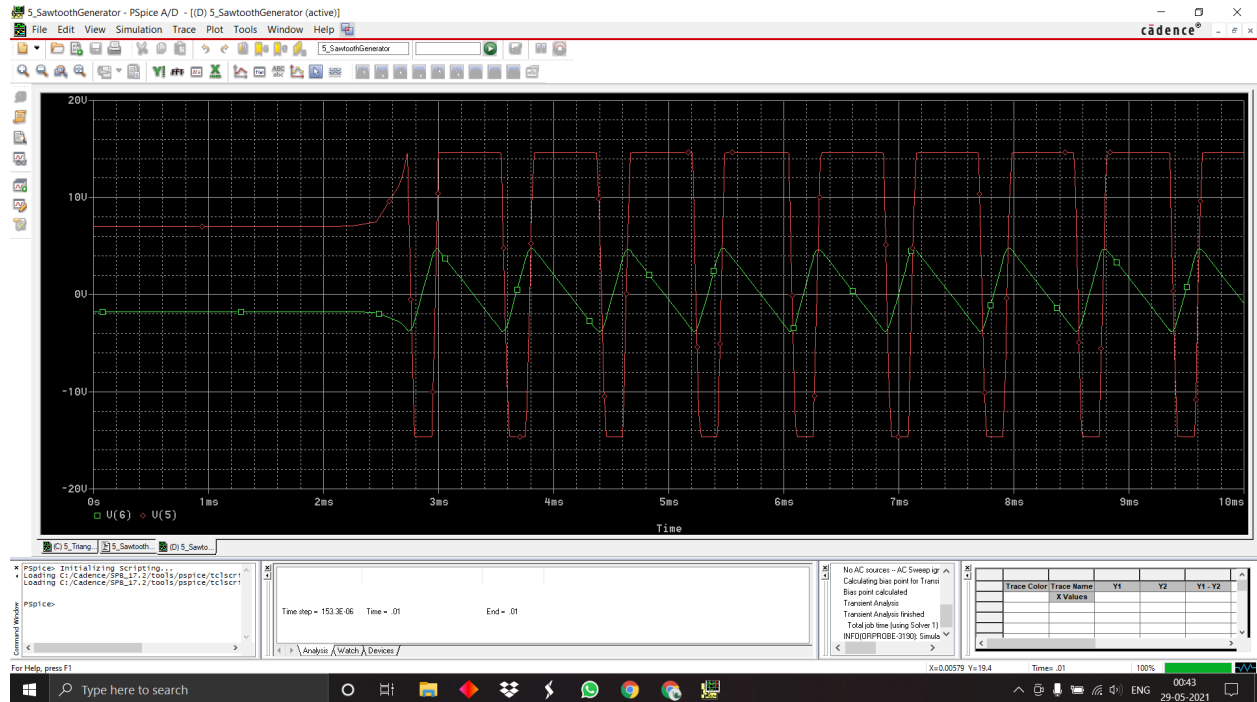

EXPERIMENT 6

Aim : To design and implement a Wein Bridge Oscillator (WBO).

a. Circuit Diagram

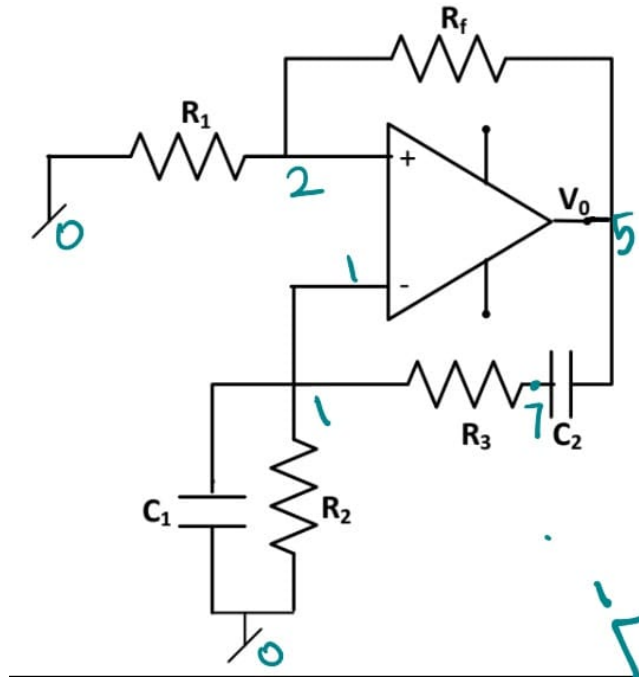

Design Procedure:

We know,

$$f_o = \frac{1}{2\pi\sqrt{R_2 R_3 C_1 C_2}}$$

Therefore, R₂ = R₃ = 10k

And C₁ = C₂ = 0.1u

b. Netlist Code

*Exp-6 Wein Bridge Oscillator (WBO)

X1 1 2 3 4 5 ua741

C1 1 6 0.1u

C2 1 0 0.1u

R1 2 0 10k

R2 1 0 10k

R3 6 5 10k


R4 2 5 20k

Vp 3 0 DC 15

Vn 0 4 DC 15

```
.ic V(1)=0 V(6)=20V
.tran 1u 0.1
```


c. Simulation

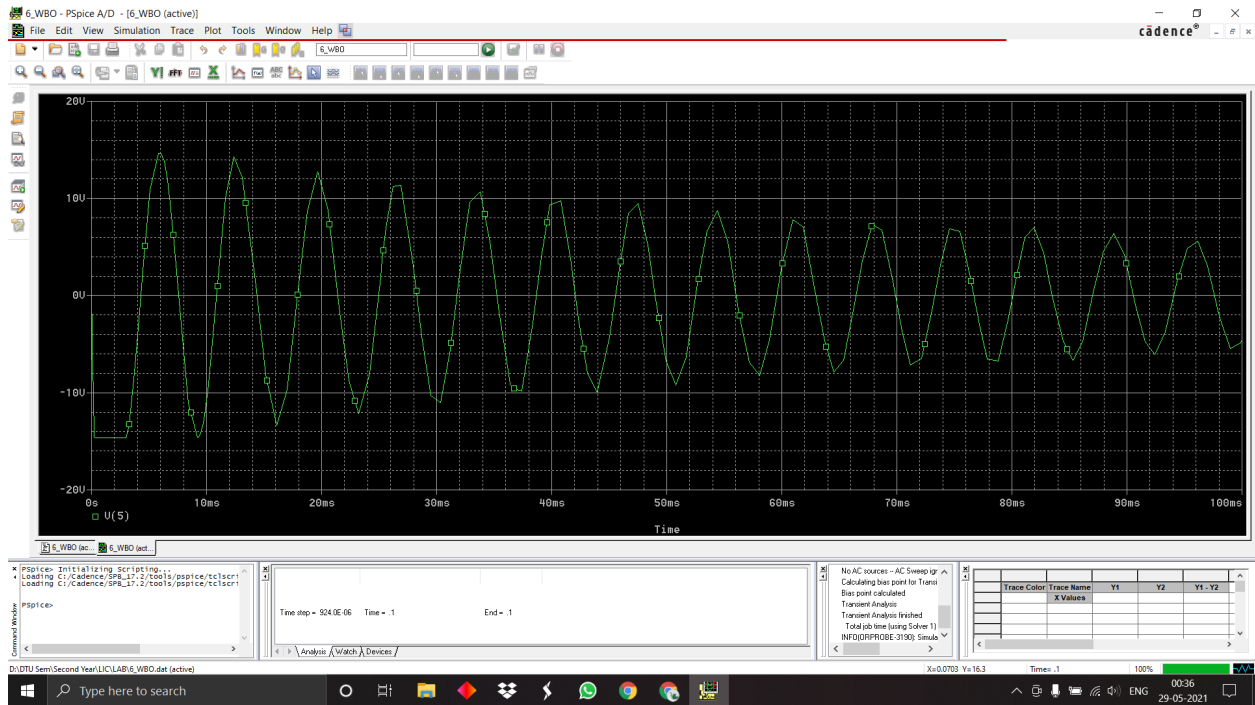

EXPERIMENT 7

Aim : Implementation of a 2nd order low pass filter.

a. Circuit Diagram

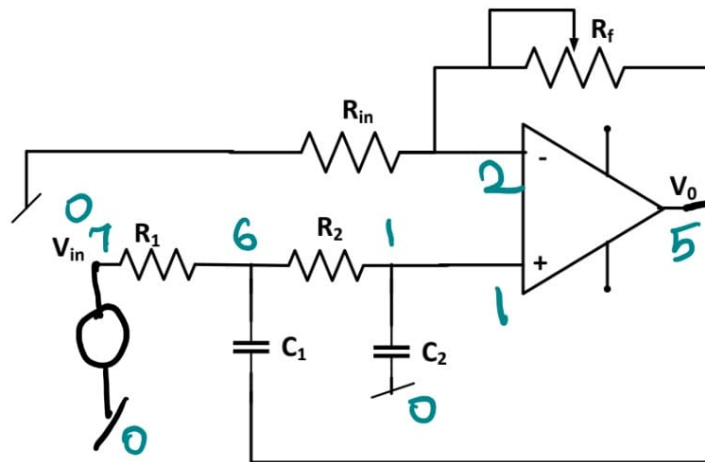

Design Procedure:

The transfer function of the circuit is given by $\frac{V_o}{V_{in}} = \frac{K\omega_o^2}{s^2 + s\frac{\omega_o}{Q} + \omega_o^2}$

Where $K = 1 + \frac{R_f}{R_1}$; $\omega_o^2 = \frac{1}{R_1 R_2 C_1 C_2}$; $Q = \frac{\sqrt{G_1 G_2}}{G_1 + G_2(2 - K)}$

For a Butterworth type of response the value of Q should be 0.707 which yields a value of K= 1.586, this gives the following relation between Rf and R1 :

$$R_f = 0.586R_1$$

If $R_1 = R_2 = 10k$, therefore $R_f = 5860$ & let $R_{in} = 10k$

And $C_1 = C_2 = 0.1\mu$

b. Netlist Code

Second Order Low Pass Filter

X1 1 2 3 4 5 ua741

V1 7 0 AC 10 sin(0 2 159)

R1 7 6 10K

R2 1 6 10K

*Rin

R3 2 0 10K

*Rf

R4 2 5 5860

```


C1 6 5 0.1uF
C2 1 0 0.1uF
Vp 3 0 DC 15
Vn 0 4 DC 15

.tran 0 50m
.ac DEC 1001 1 50k
.probe


```

c. Simulation

1) Transient Analysis

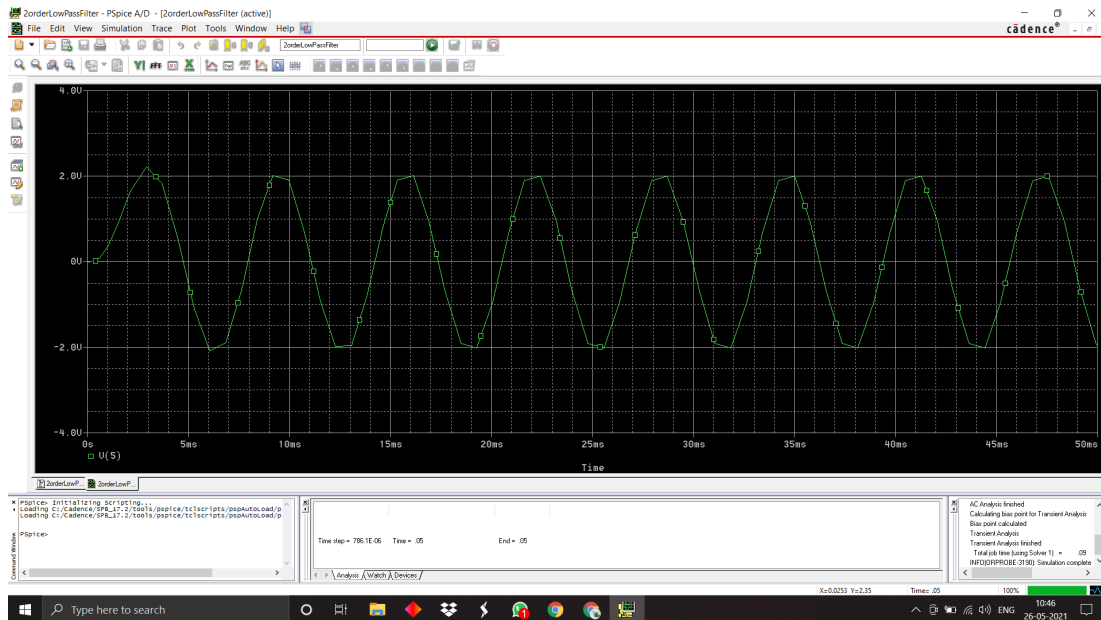


2) AC Analysis

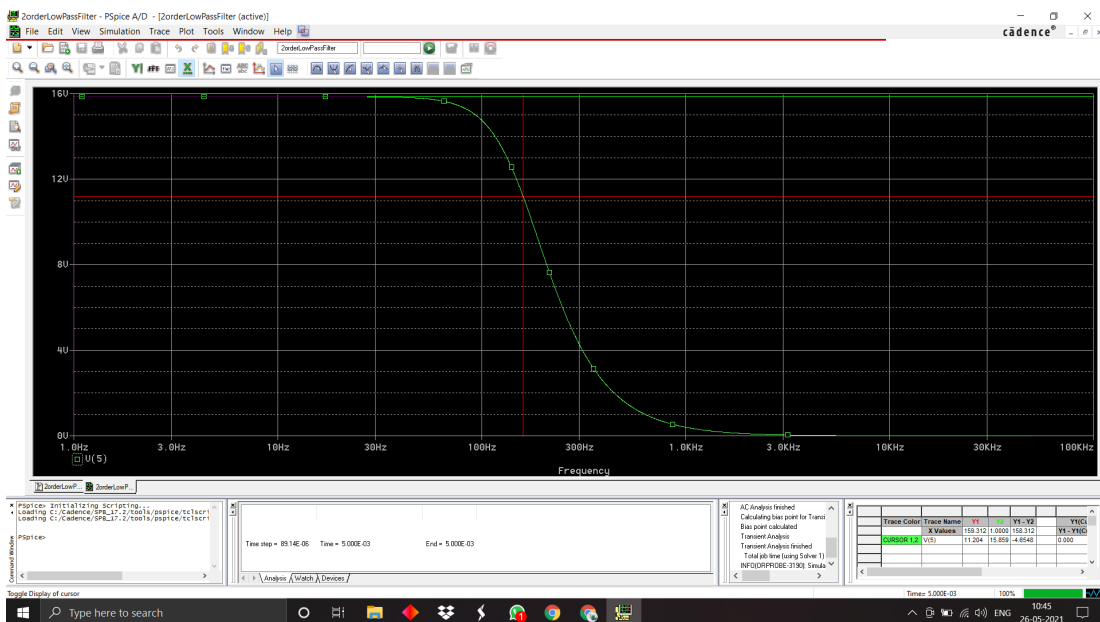

EXPERIMENT 8

Aim : Implementation of a 2nd order high pass filter.

a. Circuit Diagram

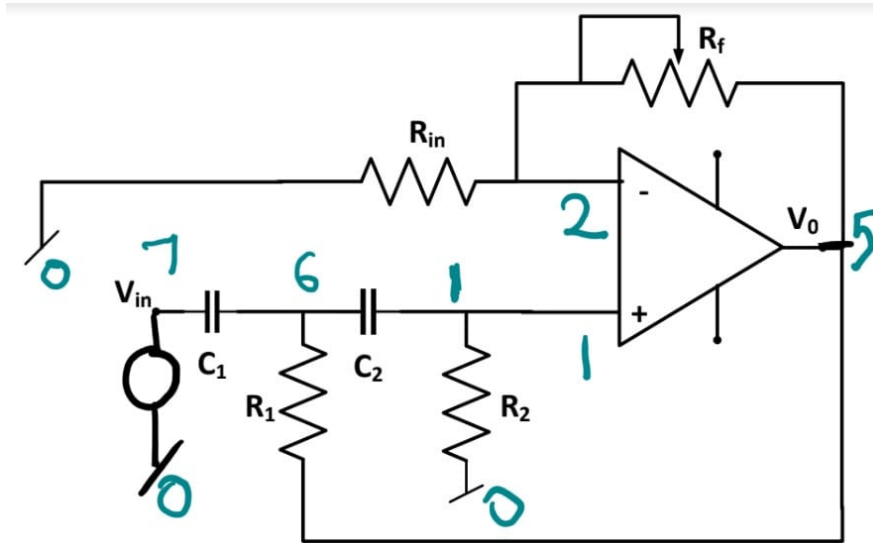

Design Procedure;

The transfer function of the circuit is given by
$$\frac{V_o}{V_{in}} = \frac{KS^2}{s^2 + s\frac{\omega_o}{Q} + \omega_o^2}$$

$$\text{Where } K = 1 + \frac{R_f}{R_1}; \omega_o^2 = \frac{1}{R_1 R_2 C_1 C_2}$$

$$Q = \frac{1}{R_1 C_1 + R_1 C_2 + R_2 C_2 (1 - K)}$$

For a Butterworth type of response the value of Q should be 0.707 which yields a value of K = 1.586, this gives the following relation between Rf and R1

$$R_f = 0.586 * R_1$$

If R1 = R2 = 10k, therefore Rf = 5860 & let Rin = 10k

And C1 = C2 = 0.1u

b. Netlist Code

```
Second Order High Pass Filter
X1 1 2 3 4 5 ua741
V1 7 0 AC 10 sin(0 2 159)
R1 5 6 10K
R2 1 0 10K
```

```


*Rin
R3 2 0 10K
*Rf
R4 2 5 5860
C1 6 7 0.1uF
C2 1 6 0.1uF

Vp 3 0 DC 15
Vn 0 4 DC 15
.tran 0 50m
.ac DEC 1001 1 50k
.probe


```

c. Simulation

1) Transient Analysis

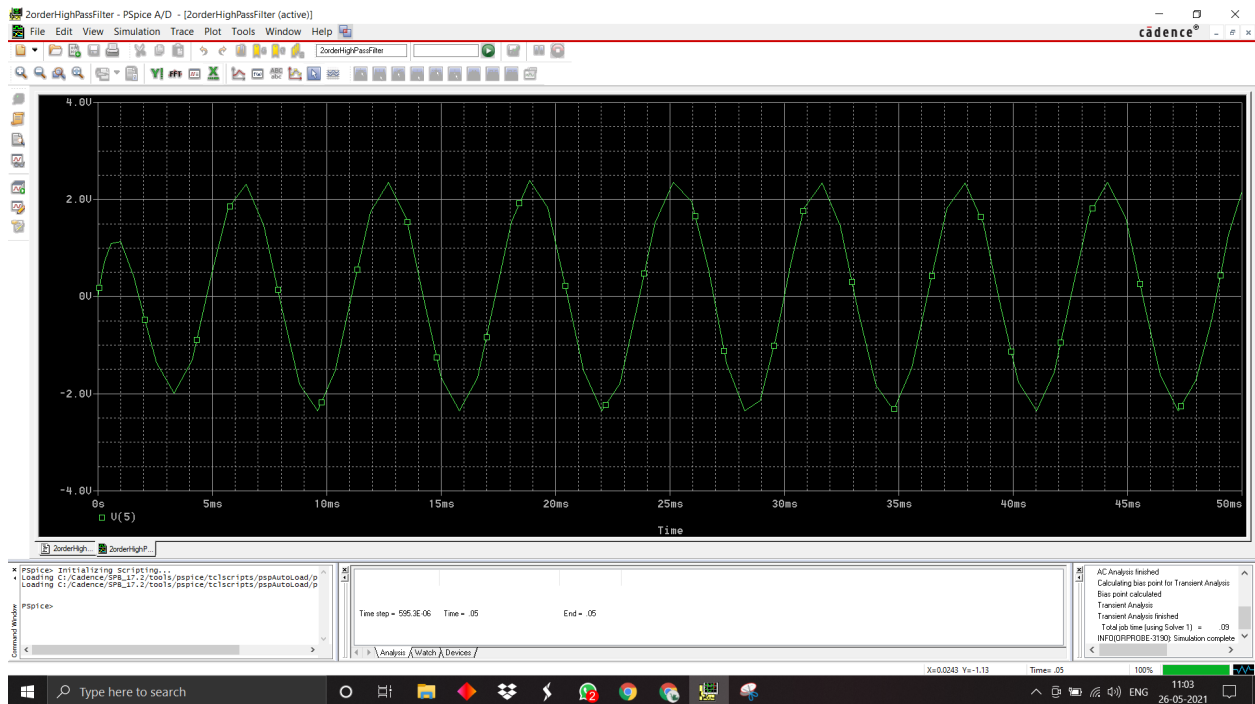


2) AC Analysis

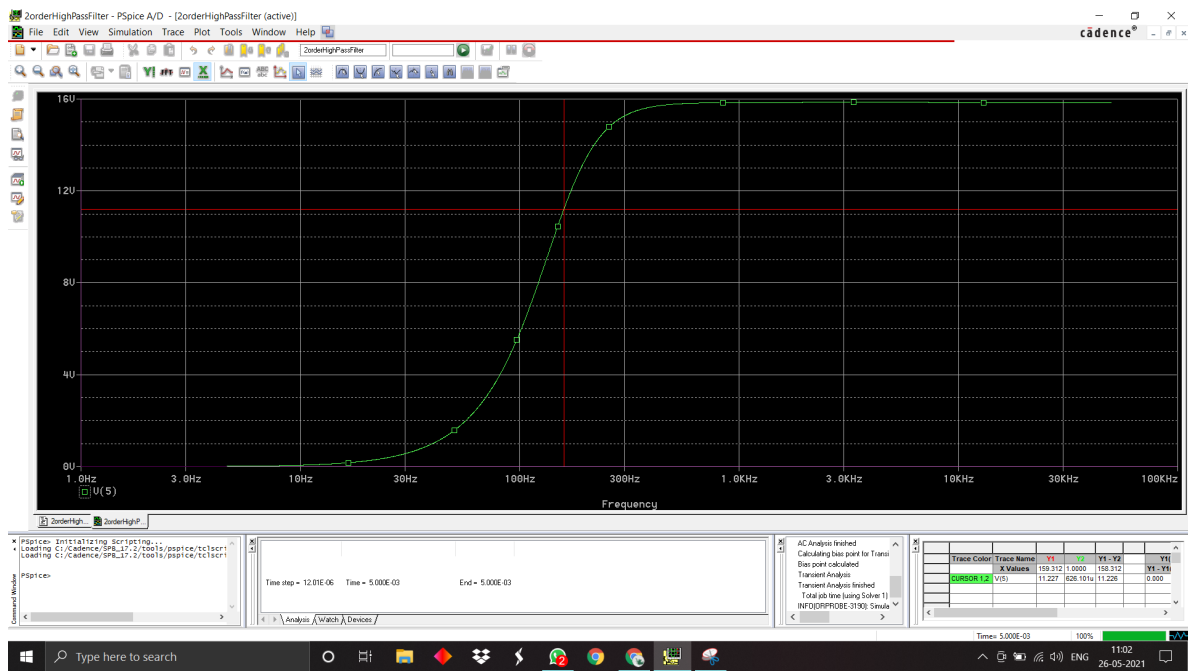

EXPERIMENT 9

Aim : To design and implement a GIC (Generalized impedance converter) based 2nd order band pass filter using $\mu A 741$.

a. Circuit Diagram

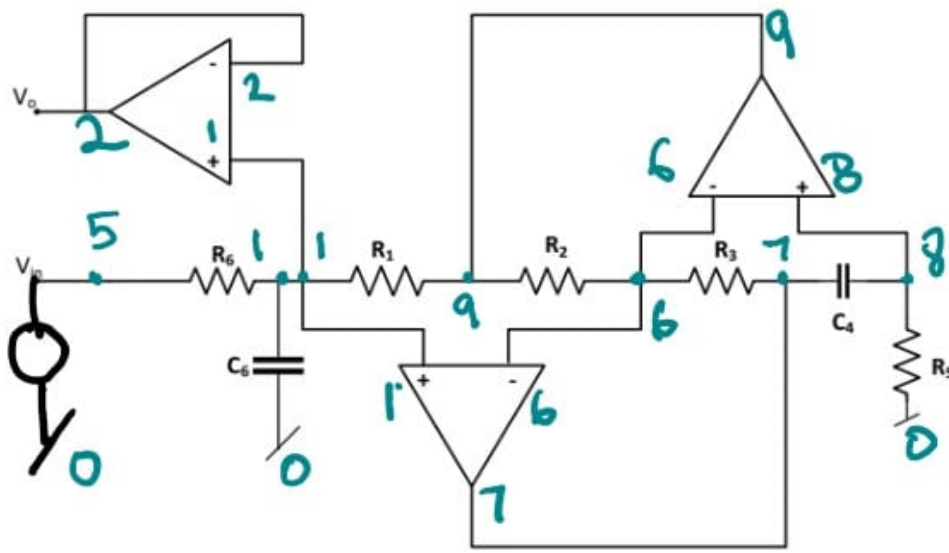

Design Procedure;

Transfer function of band pass filter can be given as:

$$T.F. = \frac{s \left(\frac{1}{CR} \right)}{s^2 + s \left(\frac{1}{CR} \right) + \frac{1}{LC}}$$

Therefore, $\omega^2 = 1/LeqC$

$$f = 1/\sqrt{2\pi LeqC}$$

$$Leq = Ra^2Ca$$

$$\omega/Q = 1/RC$$

Given: $f = 159\text{Hz}$ and $Q = 1$

$$\sqrt{LeqC} = .001$$

Let, $C = 1\mu\text{F}$

$$\text{Therefore, } Leq = 1 \rightarrow Ra^2Ca = 1$$

Let, $R_a = 10k$ therefore, $C_a = 10nF$
 For $Q = 1$, $\omega_o = 1/RC$
 Therefore, $RC = .001$
 Hence, $R = 1k\Omega$

b. Netlist Code

Second Order Band Pass Filter GIC

```
X1 1 2 3 4 2 ua741
X2 1 6 3 4 7 ua741
X3 8 6 3 4 9 ua741
V1 5 0 AC 1 sin(0 2 159)
R 5 1 1K
C 1 0 1uF
R2 1 9 10K
R3 9 6 10K
R4 6 7 10K
R5 8 0 10k
C2 7 8 10nF
Vp 3 0 DC 15
Vn 0 4 DC 15
```


```
.tran 0 65ms 45ms 65ms
```

```
.ac DEC 100 1 100mega
```

```
.probe
```

c. Simulation

1) Transient Analysis

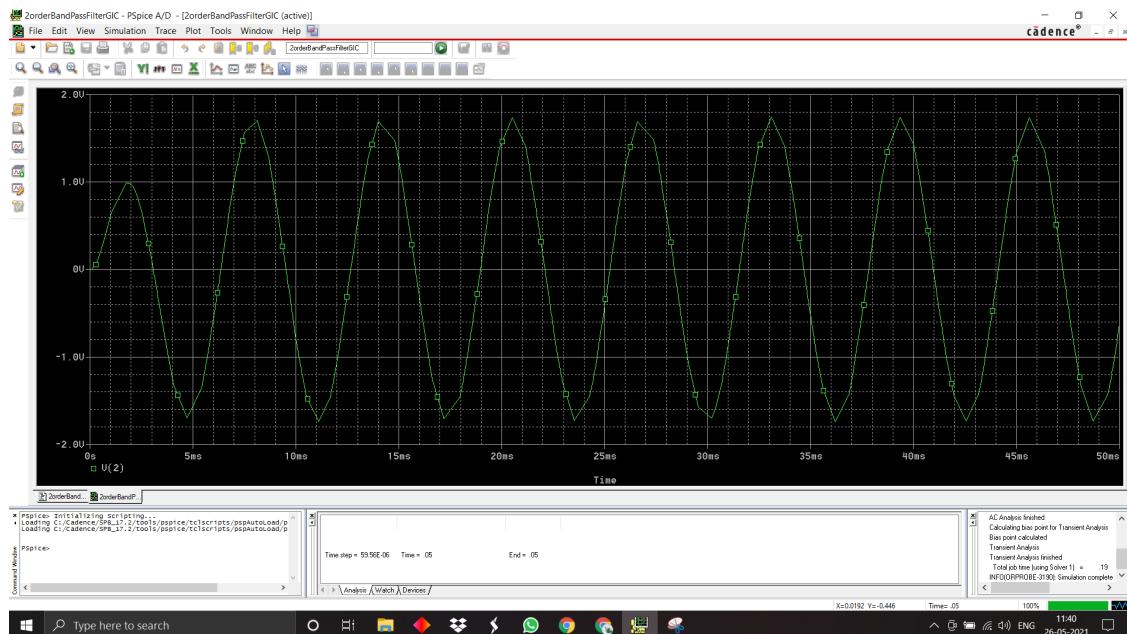

2) AC Analysis

